



Set the repeater power to high (H). This will be maximum achieved power. Solder uper schematic and connect the board between connector J1 and resistor R5 on receiver logic-R board.

Desolder R5 and solder it back only on the opposite side of J1 connector. Solder P2 to the free pad of R5 and P1 to the free side of R5. Now you can adjust 2 levels of power, low power (LPWR) and high power (HPWR).

Title		
D-STAR repeater power adjustment (2 level)		
Size	Number	Revision
A4		
Date:	12.11.2008	Sheet of
File:	C:\projekti\..D_STAR_PWR_select.SchDoc	Drawn By: S59DXX